

Input Circuit Noise Calculations for

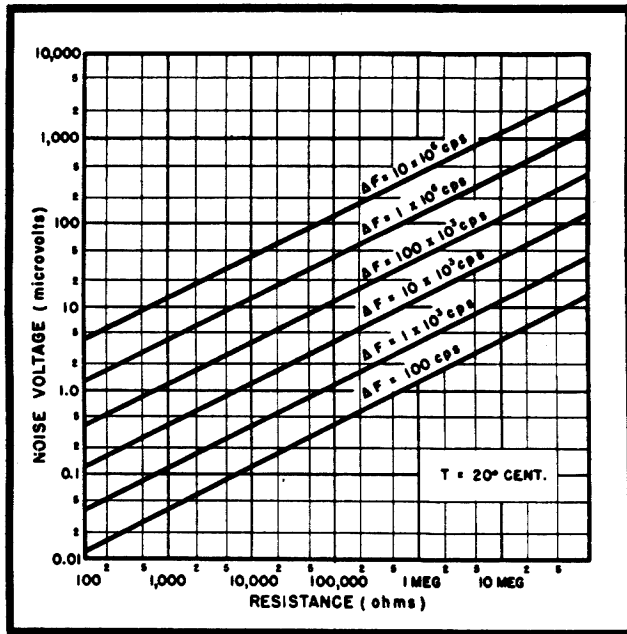


Figure 1 (below)
Sample thermal noise circuits: Frequency, 1000 kc; Q, 100; L, 300 microhenries.

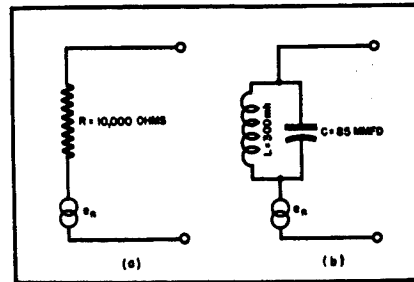


Figure 2
Thermal agitation noise voltage versus resistance and bandwidth.

MAXIMUM RECEIVER SENSITIVITY is not, in most cases, determined by the gain of the particular receiver but by the magnitude of the input circuit noise, which is generated by the antenna, the tuned input circuit, and the first tube. This is true of a-m, f-m, and television, except that in f-m and television the random noise effect assumes a far greater degree of importance than in the standard broadcast band. The reason for this is twofold:

(1) At the frequencies where these two services operate, 50 to 250 mc, the relative value of the several different noise sources assume entirely new proportions and the heretofore unimportant and little known *induced grid noise* becomes one of the predominant components of the total.

(2) Most random input and tube noise is proportional to the square root of the bandwidth. Both television, with a 4-mc band, and f-m, with a 200-kc band, occupy much wider sections of the frequency spectrum than anything previously encountered by the commercial receiver engineer.

Thermal Agitation Noise

When an alternating electric current flows through a conductor, electrons do not actually move along the conductor but they are displaced, an infinitesimal amount, first in one direction and then in the other. A voltage is built up across the conductor equal to the magnitude of the current times its resistance. Applying heat to the

conducting material agitates the molecules of the conductor and, consequently, varies the instantaneous position in space of the electrons. This random electron motion is, in a sense, a minute noise current flowing through the material and is known as *thermal agitation noise*. That is, the application of heat agitates the electron distribution of the substance thereby creating the noise.

The magnitude of the short-circuit noise current is given by

$$i_n^2 = \frac{4KT\Delta F}{R} \quad (1)$$

where:

i_n^2 = mean squared noise current (amperes²)

K = Boltzmann's Constant (joules per degree Kelvin), 1.37×10^{-23}

T = temperature (degrees Kelvin)

ΔF = bandwidth (cps)

R = resistance (ohms)

All noise currents and voltages are random fluctuations and occupy an infinite frequency band. Because of the random effect, the most convenient terminology to use in expressing their magnitude is average noise-power output. Mean-squared noise current or mean-squared noise voltage, either of which is proportional to average power, is generally used.

In the expression for various noise components the term ΔF refers to the

effective bandwidth of the circuit. This is determined from a curve of power output versus frequency by dividing the area under the curve by the amplitude of the power at the noise frequency in question. For most calculations, however, where only approximate values are desired, the bandwidth between half power points, or .707 voltage points, will give sufficient accuracy.

The equation below expresses thermal agitation noise as a voltage in series with a given resistor:

$$e_n^2 = 4KT\Delta FR \quad (2)$$

Both the above forms are true of all resistive circuit elements or combination of elements including parallel and series-tuned circuits.

Referring to Figure 1 (a), let us suppose a resistance of 10,000 ohms were connected to the input of an amplifier with a 5 kc bandwidth, i.e., 5 kc between half power points or an audio band of 2.5 kc. At room temperature, 20° C or 293° K, the terms $4KT$ in the expressions for noise simplifies to 1.6×10^{-20} , which may be used in most receiver calculations. The noise in Figure 1 (a) is therefore:

$$e_n^2 = 1.6 \times 10^{-20} \Delta FR$$

$$e_n = \sqrt{1.6 \times 10^{-20} \times 5000 \times 10,000}$$

$$e_n = 0.89 \text{ microvolt}$$

The noise bandwidth is generally determined by the narrowest element in the entire circuit under considera-

F-M And TELEVISION RECEIVERS

TRIODE AMPLIFIER	$R_{eq} = \frac{2.5}{g_m}$
PENTODE AMPLIFIER	$R_{eq} = \frac{1}{g_p + g_c} \left(\frac{2.5}{g_m} + \frac{201 g_m}{g_c^2} \right)$
TRIODE MIXER	$R_{eq} = \frac{1}{g_c} \left(g_c + \frac{g_m}{4} \right)$
PENTODE MIXER	$R_{eq} = \frac{1}{g_p + g_c} \left(\frac{4}{g_c} + \frac{201 g_m}{g_c^2} \right)$
MULTI GRID CONVERTER or MIXER	$R_{eq} = 20 \frac{1}{g_c} \left(\frac{1}{g_p} - \frac{1}{g_c} \right)$
R_{eq} = Equivalent Shot Noise Resistance g_m = Grid Plate Transconductance g_c = Conversion Transconductance I_b = Average Plate Current I_a = Average Screen Current I_c = Average Cathode Current	

Figure 3
Equivalent shot-noise resistance formulas.¹

tion. In the example for Figure 1 (b) the bandwidth of the amplifier is narrower than the tuned circuit and therefore its ΔF is used in the calculations.

Figure 1 (b) is a simple parallel-tuned circuit where the noise generating resistance is equal to the tuned circuit impedance. Again let us assume the bandwidth to be five kc per second.

$$R = Q(\omega L) = 100 \times 1900 = 190,000 \text{ ohms}$$

$$\bar{e}_n^2 = 1.6 \times 10^{-20} \Delta F R$$

$$e_n = \sqrt{1.6 \times 10^{-20} \times 5,000 \times 190,000}$$

$$e_n = 3.9 \text{ microvolts}$$

Thermal agitation noise voltage may be calculated easily with equation (2) but by using the graph shown in Figure 2 the room temperature values may be found directly.

Shot Noise

Another important component of the total receiver noise is known as *shot noise*. This noise is generated inside the vacuum tube and is due to the random fluctuations in the plate current of the tube, or, to state it in another manner, random variations in the rate of arrival of electrons at the plate. When amplified, this noise sounds as if the plate were being bombarded with pebbles or as if a shower of shot were falling upon a metal surface, hence the name *shot noise*.

Although generated essentially in the plate circuit of the tube, which is

Efficient Design of Input Stages, a Critical Requisite in F-M and Television, Involves a Careful Consideration of Three Important Factors: Total Noise, Sensitivity and Signal-To-Noise Ratio. This Paper Discusses These Factors and Offers a Physical Concept of the Three Noise Components With Formulas and Data Necessary for Input-Circuit Calculations.

by WILLIAM J. STOLZE

Engineer, Industry Service Laboratory
R.C.A. Laboratories Division, R.C.A.

TUBE TYPE	APPLICATION	PLATE VOLTS*	SCREEN VOLTS	TRANSCONDUCTANCE MICROMHOS	EQUIVALENT NOISE RESISTANCE OHMS
6AC7	PENTODE AMPLIFIER	300	150	9,000	720
6AC7	PENTODE MIXER	300	150	2,200	2,800
6AG5	PENTODE AMPLIFIER	250	150	5,000	1,650
6AG5	PENTODE MIXER	250	150	1,250	6,600
6AG7	PENTODE AMPLIFIER	300	150	11,000	1,540
6AK5	PENTODE AMPLIFIER	180	120	5,100	1,880
6AK5	PENTODE MIXER	180	120	1,280	7,520
6AK6	PENTODE AMPLIFIER	180	180	2,300	8,800
6AT6	TRIODE AMPLIFIER	250	—	1,200	2,100
6AU6	PENTODE AMPLIFIER	250	150	5,200	2,660
6BA6	PENTODE AMPLIFIER	250	100	4,400	3,520
6BA6	PENTODE MIXER	250	100	1,100	14,080
6BE6	CONVERTER	250	100	475*	190,000
6C4	TRIODE AMPLIFIER	100	—	3,100	810
6C4	TRIODE MIXER	100	—	770	3,240
6C5	TRIODE AMPLIFIER	250	—	2,000	1,250
6C5	TRIODE MIXER	250	—	500	5,000
6J5	TRIODE AMPLIFIER	250	—	2,600	960
6J5	TRIODE MIXER	250	—	650	3,840
6J6	TRIODE AMPLIFIER	100	—	5,300	470
6J6	TRIODE MIXER	100	—	1,320	1,880
6K6	CONVERTER	250	100	350*	290,000
6SA7	CONVERTER	250	100	450*	240,000
6SB7-Y	CONVERTER	250	100	950*	62,000
6SC7	TRIODE AMPLIFIER	250	—	1,325	1,890
6SG7	PENTODE AMPLIFIER	250	125	4,700	3,100
6SG7	PENTODE MIXER	250	125	1,180	12,400
6SJ7	PENTODE AMPLIFIER	250	100	1,650	6,100
6SK7	PENTODE AMPLIFIER	250	100	2,000	11,000
6SL7	TRIODE AMPLIFIER	250	—	1,600	1,560
6SQ7	TRIODE AMPLIFIER	250	—	1,100	2,300
(*) VALUES OF PLATE VOLTAGE AND CURRENT AND SCREEN VOLTAGE AND CURRENT ARE FOR TYPICAL OPERATING CONDITIONS. (—) CONVERSION TRANSCONDUCTANCE - MICROMHOS					

Figure 4
Approximate calculated equivalent noise resistance of various receiving-type tubes.

not a convenient reference point for sensitivity or signal-to-noise ratio calculations, the shot noise is nearly always referred to as a noise voltage in series with the grid. Since the following equation is true,

$$e_s = \frac{i_p}{g_m} \quad (3)$$

where

e_s = a-c grid voltage,
 i_p = a-c plate current, and
 g_m = transconductance,

by simply dividing the noise current in the plate circuit by the transconductance of the tube the shot noise may be referred to the grid and expressed in terms of grid voltage.

Another step is taken, however, to simplify the noise nomenclature. Suppose a given tube has a shot noise equal to e_n microvolts in series with its grid. It is perfectly valid to imagine that this voltage could be replaced by a resistance whose thermal agitation noise is equal to e_n (the shot noise) and consider the tube to be free of noise. This imaginary resistance, which when placed in the grid of the

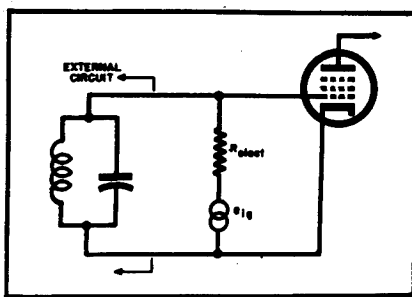


Figure 5
Position of induced grid noise in vacuum-tube circuit.

tube generates a voltage equal to the shot noise of the tube, is known as the shot noise equivalent resistance of the tube. The advantage of this terminology is that when the equivalent noise resistance of the particular tube is known, the noise volts may be calculated directly for any given bandwidth by substituting values in the following formula:

$$e_n^2 = 4 K T \Delta F R_{eq} \quad (4)$$

W. A. Harris, *Fluctuations in Vacuum Tube Amplifiers and Input Systems*, RCA Review; April 1941.

where R_{eq} = equivalent noise resistance or at room temperature

$$e_n^2 = 1.6 \times 10^{-20} \Delta F R_{eq} \quad (5)$$

If the noise were expressed as a voltage or current its value would be correct only for one particular bandwidth.

By knowing the R_{eq} of any two given tubes their relative shot noise merit is also known regardless of what bandwidth they are to operate at, while if the noise voltages were given alone the operating bandwidth at which the calculation was made would also have to be noted if the relative merits of the two tubes were to be defined.

Noise-equivalent resistance values for a number of different tube types (triodes, pentodes, and converters) and for various circuit applications (amplifiers and mixers) can be calculated by applying the expressions presented in the chart, Figure 3.¹

When the term converter is used it refers to a tube that is used for frequency conversion where the single

(Continued on page 44)

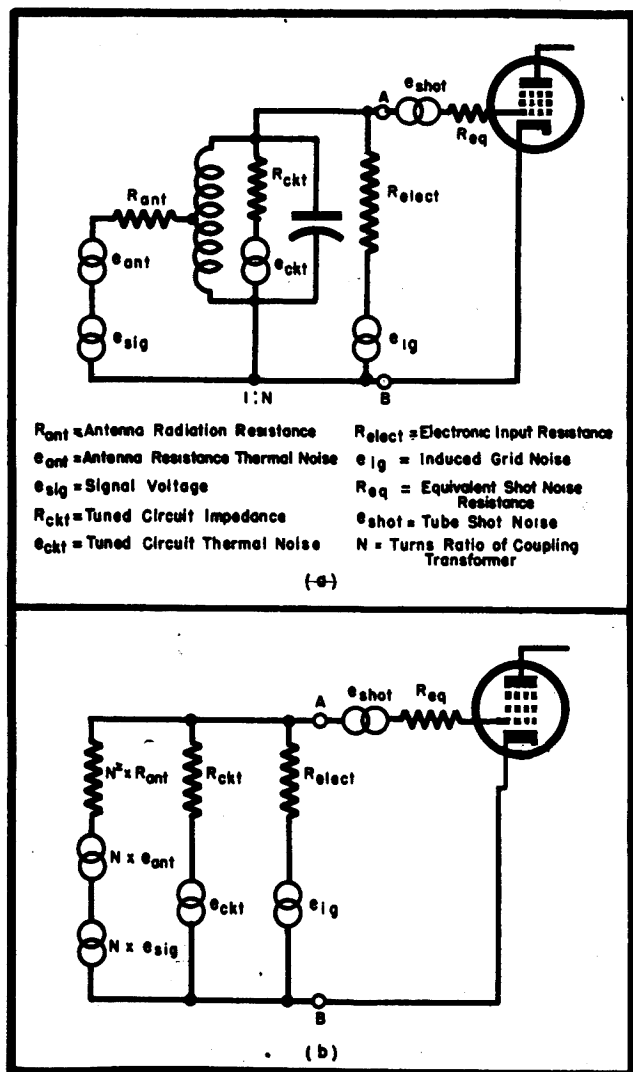


Figure 6 (below)
Approximate electronic input resistance versus frequency.


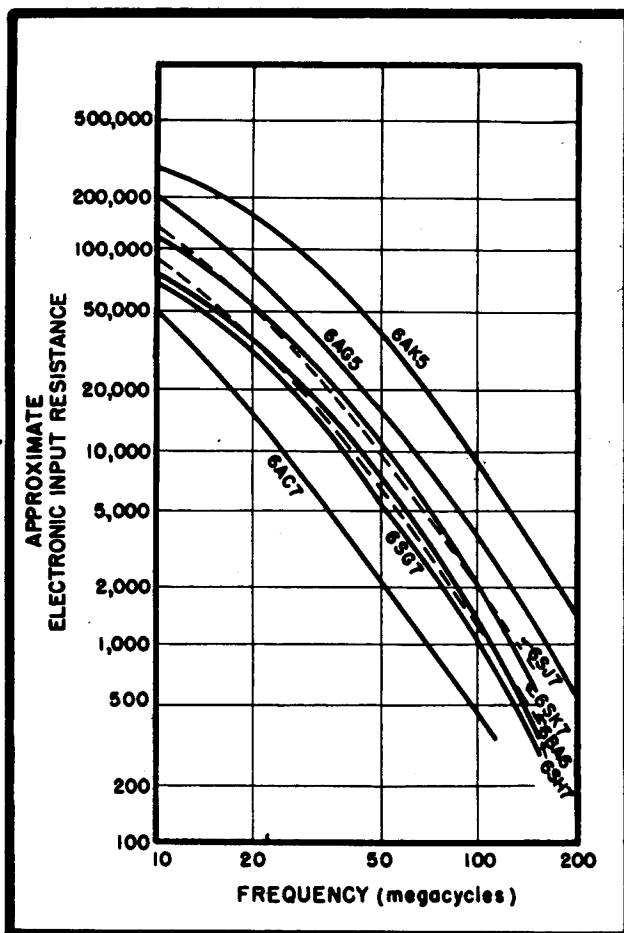


Figure 7
Position of various noise sources in input circuit.


*Laboratory
Standard*

By
**MEASUREMENTS
CORPORATION**

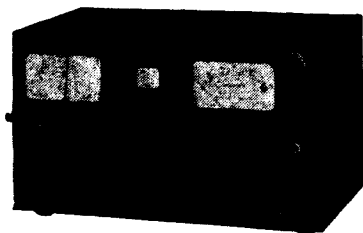

**U. H. F. RADIO NOISE and
FIELD STRENGTH METER
Model 58**

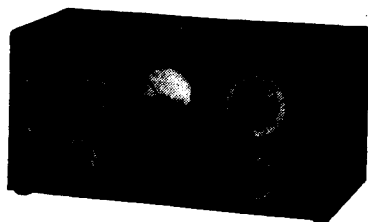FREQUENCY RANGE: 15 to 150 mc. Push-button switching for rapid, accurate measurement of noise levels or field strength.



**SQUARE WAVE
GENERATOR Model 71**

FREQUENCY RANGE: 5 to 100,000 cycles.
WAVE SHAPE: Rise time less than 0.2 microseconds.

OUTPUT VOLTAGE: 75, 50, 25, 15, 10, 5 peak volts fixed; 0-2.5 volts continuously variable.

MANUFACTURERS OF
Standard Signal Generators
Pulse Generators
FM Signal Generators
Square Wave Generators
Vacuum Tube Voltmeters
UHF Radio Noise & Field
Strength Meters
Capacity Bridges
Megohm Meters
Phase Sequence Indicators
Television and FM Test
Equipment

Catalog
on
request

**MEASUREMENTS
CORPORATION**
BOONTON NEW JERSEY



F-M/TELEVISION RECEIVERS

(Continued from page 15)

tube acts as the local oscillator and the mixer (6SA7); the term mixer where two tubes are used, one as the mixer (6SG7), and one as the local oscillator (6C4).

After the equivalent noise resistance is known the value of rms noise voltage at the grid of this tube can be calculated by applying the same expression that is used for thermal agitation noise,

$$e_n^2 = 1.6 \times 10^{-20} \Delta F R \quad (2)$$

or by using the graph of Figure 2.

Figure 4 presents calculated equivalent noise resistance values for a number of commonly used tubes acting as various types of circuit elements. These are, of course, approximate figures.

It can be seen from Figures 3 and 4 that the noise resistance or voltage is at a minimum for a triode, increasing for the pentode and the multigrid tube, following in that order.

Shot noise is unique among the noise sources in the sense that the shot-noise voltage should be considered to exist in series with the grid inside the tube. The reason for this is that nothing can be done to the external grid circuit that will alter the magnitude of this component. Even though the shot noise must be tolerated, its effect can be minimized by designing the input circuit for maximum signal at the grid. This does not reduce the magnitude of the noise but does improve the signal-to-noise ratio of the receiver.

Induced Grid Noise

Also present in the receiving tube is a third source of noise which is generated internally in the tube but whose magnitude and effect are determined partially by the external input circuit. Known as *induced grid noise*, this minute current is induced in the grid wires of the tube by random fluctuations in the plate current. It is known that a varying electron beam will induce a current in any nearby conductor. Therefore, the fluctuating plate current which is in a sense a varying electron beam, will induce a noise current in the nearby grid conductors.

The input impedance of a vacuum tube has a reactive and a resistive component. At relatively low frequencies the resistive component is very high (below about 30 mc); as the frequency is increased the resistive com-

**JONES 300 SERIES
PLUGS and SOCKETS**



P-306-CCT



S-306-AB

A high quality line of small Plugs and Sockets adaptable to a thousand uses.

All Plugs and Sockets are Polarized. "Knife-switch" Socket contacts are of phosphor bronze, cadmium plated. Bar type Plug contacts are of brass, silver plated.

Insulation is of BM 120 molded Bakelite. Caps are of metal with formed fibre linings. Made in 2 to 33 contacts. Although designed for 45 volts at 5 amperes, these Plugs and Sockets can be used at higher ratings where circuit characteristics permit. 2 contact round, others rectangular. For additional information write today for catalog No. 14 showing complete line of Electrical Connecting Devices.

HOWARD B. JONES DIVISION
CINCINNATI, OHIO
2460 W. GEORGE ST. CHICAGO 18

**JOBBERS! QUANTITY BUYERS!
SAVE MONEY**

with MID-AMERICA'S
Sensational
Values!

**FREE MONTHLY
BULLETINS**

REFLAYS
CONDENSERS
TRANSFORMERS
METERS • SWITCHES

**MID-AMERICA
Bargains**

Here's proof of the BIG BARGAINS in radio parts and electronic equipment MID-AMERICA offers EVERY MONTH to qualified quantity buyers through special bulletins and flyers. Check the outstanding buys listed here against what you've been paying—then get MID-AMERICA's FREE CATALOG and big MONTHLY BARGAIN BULLETINS!

5" Dynamic Speaker, 450 ohm field, hum bucking coil, double shielded 50 L transformer (lots of 20) \$2.95 ea. ELECTROLYTIC CONDENSERS with straps; 50/50 mfd—150 VDCW (lots of 100) 50c ea. 10 mfd—500 VDCW 1" Dia. Mallory PF (lots of 100) 78c ea. ALUMINUM CONDENSER; 4 mfd—600 VDCW oil filled paper, 4 1/2" high x 1 1/2" dia., equiv. to 8 mfd—600 VDCW electrolytic; (lots of 100) 78c ea. DPDT ROTARY RADIO-PHONO BAND SWITCH, 1/2" shank 1 1/2" shaft (lots of 100) 36c ea. ALLIANCE PHONO MOTOR, rim drive with 9" turntable (lots of 6) \$3.75 ea. ASTATIC HIGH FIDELITY PHONO PICKUP with Astatic L-72-A xtal (lots of 25) \$1.95 ea. 50L6 GT TUBES, std. brands (lots of 500) 70c ea.

For LOWER PRICES on LARGER QUANTITIES than these listed here write, wire

MID-AMERICA'S store address, Dept. R-27.
MID-AMERICA CO. Inc.
STORE: 2412 S. MICHIGAN AVE. CHICAGO 16, ILL.
WAREHOUSE: 2307 S. ARCHER AVE. CHICAGO 15, ILL.

ponent decreases and its magnitude eventually becomes comparable to or even lower than the external grid circuit impedance. The resistive component is composed of two parts, the portion due to transit time effect, and the portion due to the inductance of the cathode lead.

An expression for induced-grid noise² for tubes with control grid adjacent to the cathode follows:

$$\bar{P}_{i.g.} = 1.4 \times 4 K T_K \Delta F G_{elect}$$

or when expressed in the form of a voltage generator,

$$\bar{e}_{i.g.}^2 = 1.4 \times 4 K T_K \Delta F R_{elect} \quad (6)$$

where: T_K = cathode temperature (degrees Kelvin)

G_{elect} = electronic (transit time) component of input conductance

R_{elect} = electronic component of input resistance

From equation (6) it can be seen that the induced grid noise is proportional to the electronic or transit time component of the input resistance. Measurement of the total input resistance is a comparatively simple matter with the use of a high frequency Q meter, but the separation of the electronic and the cathode inductance components, which are essentially two resistances in parallel between the grid and ground, is a very difficult matter. Since most high-frequency tubes are constructed with either two cathode leads or one very short lead, assuming the total measured input resistance to be electronic would not introduce too great an error. Another factor in favor of this approximation is that it would be the case for maximum induced grid noise and any error introduced would more than likely be on the safe side.

Cathode temperature in most receiving tubes, which almost exclusively use oxide-coated cathodes, is approximately five times the normal room temperature in degrees K. Equation (6) can be rewritten therefore as

$$\bar{e}_{i.g.}^2 = 5 \times 4 K T \Delta F R_{elect} \quad (7)$$

where: T = room temperature (degrees Kelvin), or when $T = 300$ degrees Kelvin

$$\bar{e}_{i.g.}^2 = 8 \times 10^{-20} \Delta F R_{elect} \quad (8)$$


In circuit calculations this noise is essentially in series with a resistance

(Continued on page 46)


²D. O. North, *Fluctuations Induced in Vacuum-Tube Grids at High Frequencies*, Proc. IRE, Feb. 1941.

Dependable MICROPHONE PLUGS by CANNON ELECTRIC

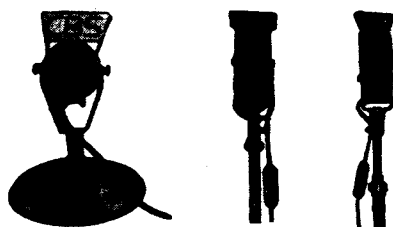Judy Canova, radio star, broadcasting over NBC in Hollywood, with Hal Gerard and Joe Kearns. RCA microphone is equipped with Types "O" or "P". ALL RADIO NETWORKS USE CANNON MICROPHONE PLUGS.





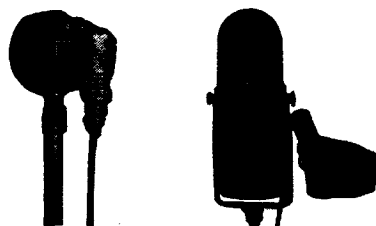Left: Type "O3-42" Receptacle and "O3-11" Plug on Western Electric table type mike used by Columbia Broadcasting Co. Center and Right: Other large network mikes use type "O" for cable extension. The latchlock device prevents accidental disconnection resulting from jerks or strain on cord.



Left: Microphone with "P-42" Receptacle and P-CG-11 Plug used for platform public address. (Photo courtesy Reiss P. A. Systems, Detroit). Right: Mike used by CBS-Hollywood, with P-CG-12 plug shown in hand. As in the case of the above Type "O", two mating "P" plugs can be used conveniently for cable extension where receptacle is not an integral part of the microphone itself.

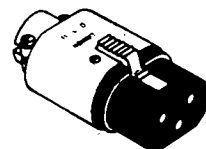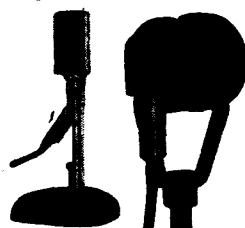The New lightweight Type "XL" is standard equipment on the equally new RCA "Announce" Microphone which has a unique construction in the stem, allowing the plug to swing into the stem with a cover. Relief spring on XL-3-11 plug protects cord from sharp bends. Adapters are available to users of microphones such as the Turner (second to right) for those desiring to convert to Cannon "XL" Plugs.




TYPE "O"

Two plugs and six receptacle styles available in this series. One oval insert arrangement with three 30-amp. contacts for No. 10 B&S stranded wire.




TYPE "P"

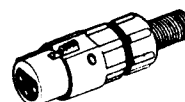Five plugs and nine standard receptacle styles available in six insert arrangements; two to six 30-amp. contacts, one eight 15-amps. for No. 14 B&S stranded wire.



TYPE "XL"

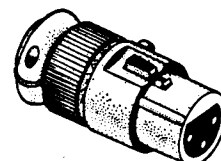Two small plugs and four receptacles with zinc shells carry three 15-amp. contacts for No. 14 B&S stranded wire. Equipped with compression gland and relief spring.



TYPE "XL"

Two steel shell XL plugs for rough, heavy-duty usage. Same insert arrangement as above. Integral clamp construction and leading XL features.

Write Dept. B-121 for C-46A Condensed Catalog, describing all above connectors and list prices. Available from jobbers everywhere.



CANNON ELECTRIC DEVELOPMENT COMPANY


3209 Humboldt Street, Los Angeles 31, California

Canada & British Empire - Cannon Electric Co., Ltd., Toronto, Ontario • World Export Agents (excepting British Empire) - Frazar & Hansen, 301 Clay St., San Francisco 11, Calif.

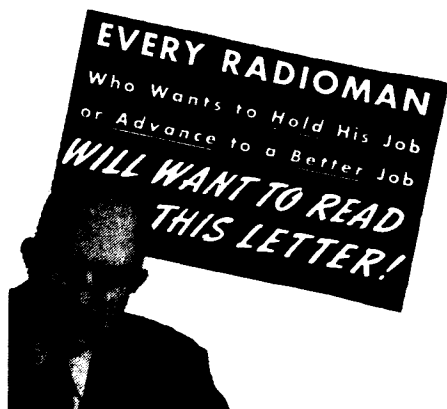E. H. Rietzke, President of CREI, invites
You to Write for this

Free

Significant Analysis of Job Opportunities in Radio Electronics



The Story Behind This Interesting Letter You Will Want to Read . . .

Our advertising agents, realizing that vital changes are taking place in the radio industry, asked me to give them a factual report of the unprecedented job opportunities created by the almost unbelievable expansion of the radio industry.

My letter to them contains some pertinent viewpoints on the subjects of **COMPETITION — INDUSTRY EXPANSION — OPPORTUNITIES**. These are first-hand observations based on my own experiences . . . a great deal of time spent in the field and constant contact with leaders in the radio industry.

The immediate reaction of our agency upon reading this letter was that it contained so much inspiration and information that it should be reproduced for thousands of radiomen to read. Therefore, this unusual advertisement to invite you to send for, and read, this letter.

It is doubtful if many radiomen realize the actual things that are happening. That is why I think you will want to read this letter. You are invited to send for your personal copy today.

E. H. Rietzke
President, CREI

**CAPITOL RADIO
ENGINEERING INSTITUTE**
Washington 10, D. C.

MAIL COUPON FOR FREE COPY. NO OBLIGATION

Capitol Radio Engineering Institute
16th and Park Road, N. W., Dept. CO-2
Washington 10, D. C.

Gentlemen: Please send me FREE, Mr. E. H. Rietzke's Analysis of Job Opportunities in Radio-Electronics.

NAME
POSITION..... AGE.....
ADDRESS
CITY..... ZONE..... STATE.....

(Continued from page 45)

equal to R_{elect} located between the grid and ground; Figure 5.

The approximate input resistance for a number of common receiving tubes in the frequency range of f-m and television is given in Figure 6. This chart can be used to find approximate input resistance values for induced grid-noise calculations.

Total Noise Calculations

Calculations of total input noise are made by using the grid of the input tube as a reference point. There are many sources of noise and each must be calculated and referred to the grid reference point before a summation is made. Since noise is a random effect and calculated on a power basis, the separate components cannot be added directly but as the square root of the sum of the squares.

$$\text{Total Noise} = \sqrt{e_a^2 + e_s^2 + e_g^2 + \text{etc.}} \quad (9)$$

The various noise voltages that must be referred to the first grid are:

- (1) Thermal agitation noise of the antenna radiation resistance.
- (2) Thermal agitation noise of the tuned grid circuit.
- (3) Shot noise of the input tube.
- (4) Induced grid noise of the input tube.
- (5) Grid circuit noise of the following stages referred back to the first grid.

In Figure 7 (a) appears a diagram of a practical input circuit and the location of all the circuit parameters and noise voltages. Figure 7 (b) is essentially the same except that the antenna circuit is reflected through the transformer and considered to exist at the grid. This is the diagram that is most useful in calculating the total input circuit noise.

The steps necessary to find specific values for each of these factors are shown in Figure 8. Antenna radiation

(Continued on page 48)


Figure 8

Procedure for calculating various noise voltages.

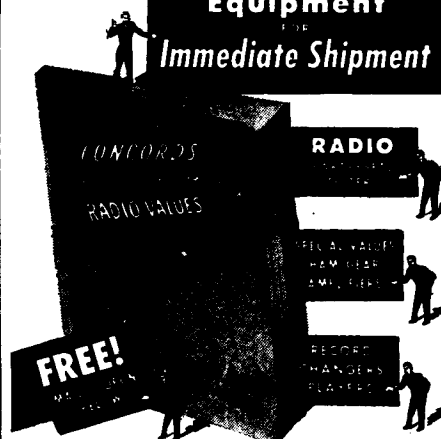- (1) R_{ant} — Depends upon specific antenna
- (2) $e_a = \sqrt{1.6 \times 10^{-20} R_{\text{ant}} \Delta f}$ — or directly from Fig. 2
- (3) $R_{\text{ckt}} = Q \omega L = \frac{Q}{\omega C}$
- (4) $e_{\text{ckt}} = \sqrt{1.6 \times 10^{-20} R_{\text{ckt}} \Delta f}$ — or directly from Fig. 2
- (5) R_{elect} — From accompanying chart, Fig. 6
- (6) $e_g = \sqrt{8 \times 10^{-20} R_{\text{elect}} \Delta f}$
- (7) R_{eq} — From accompanying chart, Fig. 4
- (8) $e_{\text{sig}} = \sqrt{1.6 \times 10^{-20} \Delta f R_{\text{eq}}}$ — or directly from Fig. 2

*Just
Out!*

CONCORD
Bargain Catalog of
RADIO
Equipment
Immediate Shipment



THOUSANDS OF ITEMS! OUTSTANDING VALUES!

Just off the press—48 exciting pages of radio parts, equipment, and supplies for dealers, servicemen, amateurs, maintenance, testing, building and experimenting—Thousands of items **NOW IN STOCK** and ready for **IMMEDIATE SHIPMENT!** Big feature sections of Radio Sets, Communications Receivers, Amplifiers, Replacement Parts, Ham Gear, Record Players and Portables, Record Changers and complete Sound Systems. Page after page of bargains in top-quality standard-make radio parts and electronic equipment.

Mail Coupon NOW for FREE COPY

Mail coupon below **TODAY** for your **FREE COPY** of this latest Concord Buying Guide and Bargain Catalog of Radio needs you can order for **SAME DAY SHIPMENT** from complete stocks in Chicago and Atlanta.

CONCORD


RADIO CORPORATION
LAFAYETTE RADIO CORPORATION
CHICAGO 7, ILL. ATLANTA 3, GA.
901 W. Jackson Blvd. 265 Peachtree St.

CONCORD RADIO CORP., Dept. R-27
901 W. Jackson Blvd., Chicago 7, Ill.

Yes, rush **FREE COPY** of the new Concord Bargain Catalog.

Name.....
Address.....
City..... State.....

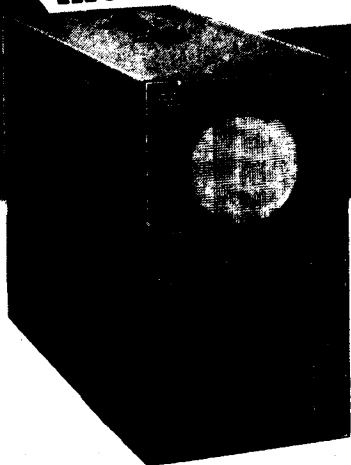NEW! ELECTRONIC DEVELOPMENT 5" OSCILLOSCOPE



STOCK
NO.
84-376

ONLY
\$99⁵⁰

This new 5" Cathode Ray Oscilloscope is a precision instrument at an attractively low price, designed for practical application in laboratory research and production work. Sturdily built to stand up under continuous use, and ably engineered for accuracy, versatility and easy operation. Has wide frequency range, 10 cycles to 300 Kc. Deflection sensitivity, 1 volt RMS per inch. Sweep range, 10 cycles to 60 Kc. in four steps. For 110-120 volt, 50-60 cycle operation. In welded steel cabinet, with baked black wrinkle-finish; 8½" wide, 14½" high, 18½" deep. Instrument panel in black, with white designations; has removable calibrated plastic scale. Complete with tubes. No. 84-376. Net Only. \$99.50

Order from the Central Source
for Everything in Radio and Electronics

ALLIED RADIO CORP.

833 W. Jackson Blvd., Dept. 31-B-7, Chicago 7, Illinois

Send for

ALLIED

Catalog
No. 111

(Continued from page 46)
tion resistance varies widely with the type of antenna chosen, but for f-m and television work it is generally in the order of 75 to 300 ohms. When the noise is known in terms of an equivalent resistance, as is the case here for the antenna, tuned circuit, and shot noise, the equivalent voltage can be either calculated or obtained directly from Figure 2.

In order to add the antenna, tuned circuit, and induced grid noise to the shot noise the effective voltage of these three components at the grid, or between the points A and B, must be known. Each must go through what is essentially a resistive divider and may be calculated as shown in Figure 9.


After knowing the magnitude of the separate sources that exist between A-B, the total noise voltage is

$$e_{\text{total}} = \sqrt{e_{\text{shot}}^2 + (e_{\text{ant. at A-B}})^2 + (e_{\text{t-c. at A-B}})^2 + (e_{\text{ckt at A-B}})^2} \quad (10)$$

One other factor may effect this total, however. If the total noise of the following stages, which is calculated similarly, ignoring the antenna of course, is appreciable it must be added to the constants of Figure 9. In

Figure 9

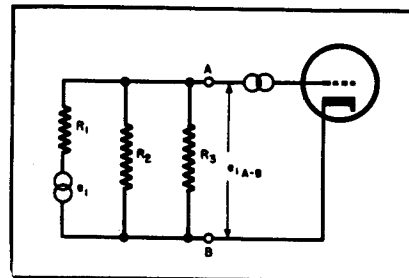Circuit for reflecting various voltages to the grid.



To find the effective voltage of the antenna, the tuned circuit, and the induced grid noise at the grid of the tube let R_1 equal one of the above noise resistances and e_1 its generated voltage. If R_2 and R_3 equal the other two noise resistances the effective voltage at the grid is

$$e_{\text{A-B}} = \frac{e_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} \times \frac{R_2 R_3}{R_2 + R_3}$$

This calculation must be performed for the three components in turn.

SPECIALIZED

CABINETS

PANELS • CHASSIS • RACKS

PAR-METAL
PRODUCTS CORPORATION
32-62 - 49th STREET
LONG ISLAND CITY 3, NEW YORK
Export Dept.: Radio International Corp.
13 East 40 Street, New York 16

The time-tested Par-Metal line presents superior features of styling, design, and construction. True to policy, Par-Metal continues to specialize in Electronic Housings exclusively...and is therefore able to offer leadership in value. Compare! Write for Catalogue.

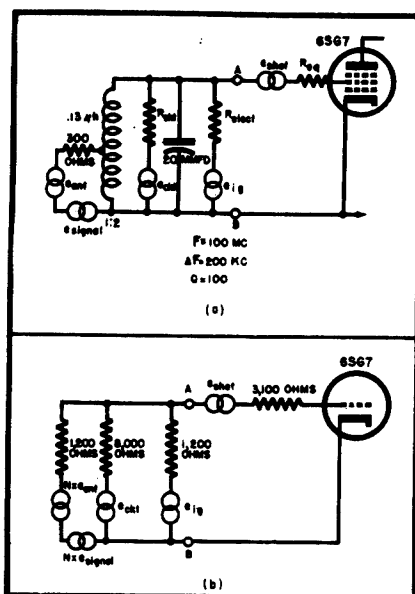


Figure 10
Typical f-m receiver input circuit.

reflecting it to the first grid the second stage noise should be divided by the gain of the first tube. When the gain is about ten or more this factor may usually be neglected.

Effective signal voltage across $A-B$ is calculated in the same way as the antenna noise in Figure 9. The signal-to-noise ratio is now also known.

Since the signal-to-noise ratio is determined by the signal strength and the total noise at the grid of the input tube, for a receiver that has a mixer, such as 6SK7, for the input tube, the signal-to-noise ratio may be considerably improved by the addition of an r-f tube, such as a 6SG7, which has considerably less total noise. By adding additional r-f tubes (6SG7s), however, since the total noise and signal at the grid will be the same, the signal-to-noise ratio will not be improved.

Sample Circuit Calculations

For a sample problem let us calculate the total noise at the grid of an f-m receiver r-f amplifier stage, assuming the circuit in Figure 10(a) to be under consideration.

As a simplification of procedure the steps in the calculation will be numbered.

- (1) $N^2 R_{ant} = 1200$ ohms (calculated)
- (2) $R_{e, tot} = 1200$ ohms (Figure 6)
- (3) $R_{ekt} = Q \omega L = 8000$ ohms (calculated)
- (4) $R_{eq} = 3100$ ohms (Figure 4)

At this point it will be convenient to redraw the circuit as shown in Figure 10(b).

- (5) $N e_{ant} = 2$ microvolts (Figure 2)



Our huge inventory of relays is, we believe, the largest and most complete in the country. These relays were made to exacting standards by America's leading manufacturers and are guaranteed in every respect. This equipment will meet your critical quality requirements and save you a large portion of the cost. Our new illustrated Relay Catalog is now ready and will be mailed upon request.


Consult Wells for Quality Radio Parts

We can make immediate delivery of a wide variety of radio components either singly or in quantity. Lists are available on the following items: Volume controls, condensers, resistors, phone jacks and plugs, wafer switches, Micro switches, transmitting tubes and Jones strips.

Army Walkie Talkies!

Here's a complete portable station for 28 to 52 Mc. operation. May be easily modified for 2 1/2 meter use. Crystal calibrator. Shipped complete with tubes, handset, telescope antenna and new battery — ready to operate — only \$45.00 each.

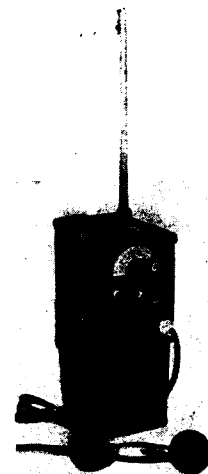Extra batteries (80 hours continuous service) \$4.75 each.



Look for the Wells Display
At Your Jobbers

4717 W. MADISON ST., DEPT M-2, CHICAGO 44, ILL.

$$(6) e_{i, g.} = \sqrt{8 \times 10^{-20} \times 200 \times 10^3 \times 1200} = 5 \text{ microvolts} \quad (\text{equation (8)})$$

- (7) $e_{ekt} = 6$ microvolts (Figure 2)
- (8) $e_{shot} = 3.5$ microvolts (Figure 2)

The next step is to find the effective voltage of each source between the grid and ground (or $A-B$) as shown in Figure 9.

$$(9) e_{ant} A-B = \frac{2}{1200 + 1040} \times 1040 = 0.93 \text{ microvolt}$$

$$(10) e_{i, g.} A-B = \frac{5}{1200 + 1040} \times 1040 = 2.3 \text{ microvolts}$$

$$(11) e_{ekt} A-B = \frac{6}{8000 + 600} \times 600 = 2.5 \text{ microvolts}$$

And the total noise is therefore

$$(12) e_{total} = \sqrt{3.5^2 + 0.93^2 + 2.3^2} = 4.9 \text{ microvolts} \quad (\text{equation (10)})$$

Conclusions

Selection of an input tube for a television or f-m receiver is dependent:

(Continued on page 51)

F-M/TELEVISION RECEIVERS

(Continued from page 49)

upon many varying circuit conditions and individual requirements. The choice of using balanced or unbalanced input, permeability or capacitor tuning, noisy pentodes or quiet triodes that possibly require neutralization, among others, lies entirely with the design engineer. Considering these reasons and various engineering and economic compromises, no particular tube can be chosen and defined as *the input tube*. Complete noise information about the circuits involved is, necessary, however, as this is one of the determining factors for good sensitivity and signal-to-noise ratio.

TRANSMITTER BUILDING

(Continued from page 43)

though it does leave some blind spots. In practice this has not been found to be objectionable.


In the rear workroom a soundproof booth was constructed to house a United Press teletype. This has also been quite adequate, but is frequently a problem in small buildings where it is necessary to place teletype equipment close to studios. This booth is constructed of celotex walls with a dead-air space and a rock wool packing. It provides about a 40-db sound transmission loss.



PROVIDE DELAYS RANGING FROM 1 TO 120 SECONDS

FEATURES:—Compensated for ambient temperature changes from -40° to 110° F... Hermetically sealed; not affected by altitude, moisture or other climate changes... Explosion-proof... Octal radio base... Compact, light, rugged, inexpensive... Circuits available: SPST Normally Open; SPST Normally Closed.

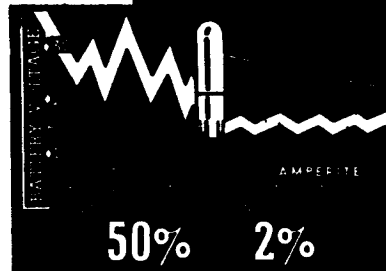PROBLEM? Send for "Special Problem Sheet" and Bulletin.



Ampelite REGULATORS are the simplest, lightest, cheapest, and most compact method of obtaining current or voltage regulation... For currents of .060 to 8.0 Amps... Hermetically sealed; not affected by altitude, ambient temperature, humidity.

Write for 4-page Illustrated Bulletin.

AMPERITE CO., 561 Broadway, New York 12, N. Y.

Manufactured by Ampelite Corp., Ltd., 16, King St. W., Toronto

HUGE STOCKS!

TRANSMITTING
AND SPECIAL
PURPOSE

TUBES

NEWARK NOW AGENTS OF WAR ASSETS ADMINISTRATION

Newark has been appointed agents of the War Assets Administration for transmitting and special purpose electronic tubes.

HUGE STOCKS! WIDE SELECTION!

This means that you can now get prompt Newark service on the previously hard-to-get tubes, priced at a fraction of their original cost. Make Newark your headquarters for tubes — whether it's for experimental work or production runs.

- ACTING AS AGENTS FOR WAR ASSETS ADMINISTRATION UNDER CONTRACT WAS(p) 7-167
- WRITE: 242-L W. 55th STREET, NEW YORK CITY

NEW YORK
Offices & Warehouse
242 W. 55th St., N.Y. 19

NEWARK TELEPHONE
ELECTRIC COMPANY INC. Circle 6-4060

New York City Stores: 115-17 W. 45th St. & 212 Fulton St.

WRITE FOR NEWARK'S LIST OF TUBES

Make Newark your source, too, for all needed radio and electronic parts. Brisk, competent service assures quick delivery.